

Arduino Mega PIR Alarm

Written By: Ethan Flubacher


PARTS:

- Arduino Mega (1)
- Parallax PIR sensor (1)
- <u>8 Ohm mini speaker (1)</u>

SUMMARY

Here's how to make a simple Arduino Mega PIR alarm.

Step 1 — Connect PIR sensor

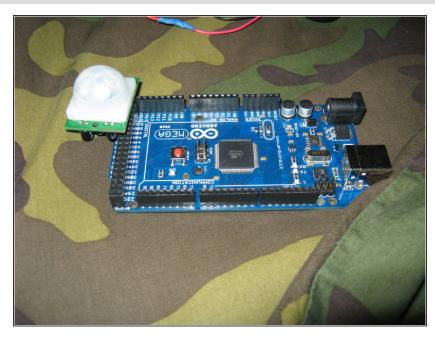


• GND to ground, V+ to pin 53, OUT to pin 51.

Step 2 — Connect speaker



Connect speaker to pin 41 and ground.

Step 3 — Upload code

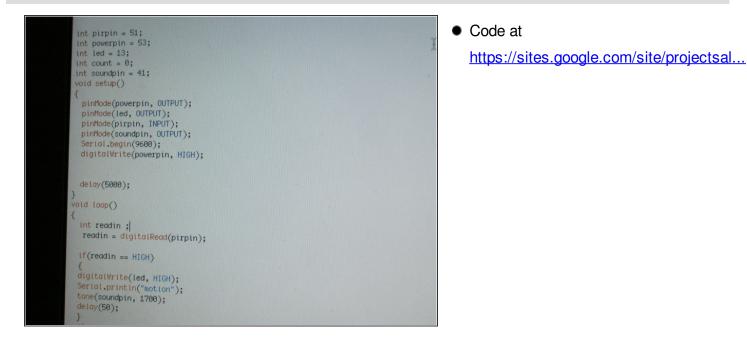

This document was last generated on 2012-11-03 03:09:25 AM.